

$$V_{\max} = \boxed{SV}$$

$$E_x = V_{\max} = S + r = \boxed{10V}$$


$$c) \quad 10 = \frac{20 \times 100}{R + 100}$$

$$R + 100 = 200$$

$$\boxed{R = 100\Omega}$$

Measurement of Low Resistance ($\sim 1\Omega$)

Kelvin's Bridge

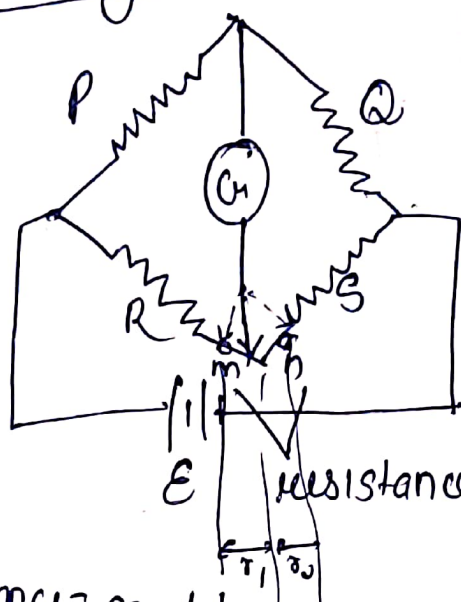

we make arrangement

$$\boxed{\frac{r_1}{r_2} = \frac{P}{Q}}$$

$$\boxed{r_1 + r_2 = r}$$

at balance condition

$$\boxed{R + r_1 = \frac{P}{Q} (S + r_2)}$$

$$\frac{r_1}{r_1 + r_2} = \frac{P}{P + Q}$$


$$R + \frac{P r}{P + Q} = \frac{P}{Q} \left(S + \frac{Q}{P + Q} r \right)$$

$$r_1 = \frac{P r}{P + Q}$$

$$r_2 = \left(\frac{Q r}{P + Q} \right)$$

$$\boxed{R = \frac{P}{Q} S}$$

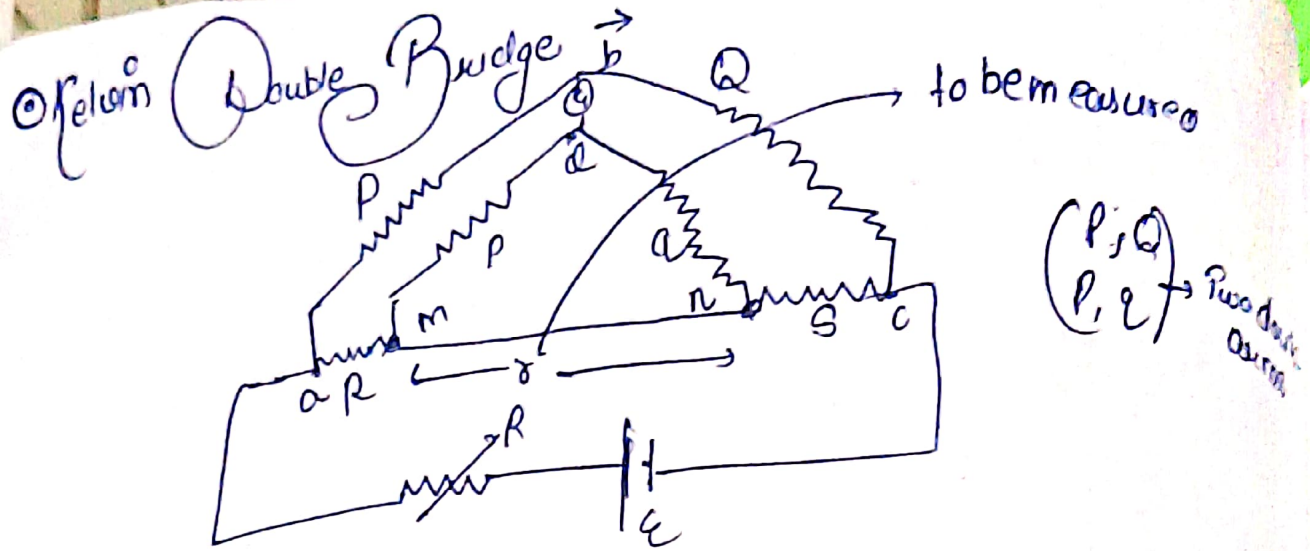involvement of r is not affecting the overall equation



$$\frac{P}{Q} = \frac{p}{q} \quad \text{if } I_g = 0$$

$$R = \frac{P}{Q} \cdot S + \left(\frac{rQ}{p} \right) \left(\frac{P}{Q} - 1 \right)$$

$$E_{ab} = \frac{P}{P+Q} E_{ac}$$

$$E_{ac} = I \left[R + S + \frac{(p+q)r}{p+q+r} \right]$$

$$= \frac{P}{Q} \cdot S + \frac{qr}{p+q+r} \left(\frac{P}{Q} - 1 \right)$$

$$E_{amd} = I \left(R + \left(\frac{(p+q)r}{p+q+r} \right) \cdot \frac{p}{p+q} \right)$$

parallel combination $\parallel p$

$$= I \left(R + \frac{pr}{p+q+r} \right)$$

In balance condition

$$E_{ab} = E_{amd}$$

$$\frac{P}{P+Q} \left[R + S + \frac{(p+q)r}{p+q+r} \right] = I \left(R + \frac{pr}{p+q+r} \right)$$

$$\boxed{R = \frac{P}{Q} S}$$

addition of another branch is not affecting bridge equation


• It is desirable to keep the value of small r as low as possible in order to minimise the error in the

Measuring High Value of resistance (MΩ)

① Loss of charge method

② Mega Ohm Bridge


1) Loss of charge method

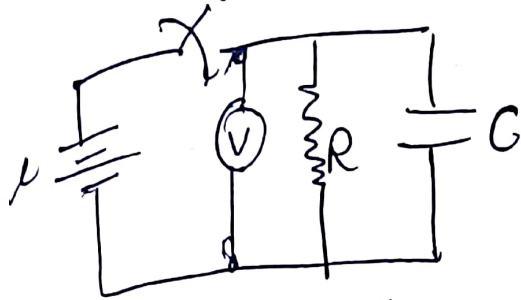

$$V = V_0 e^{-\frac{t}{RC}}$$

$$\frac{V}{V_0} = e^{-\frac{t}{RC}}$$

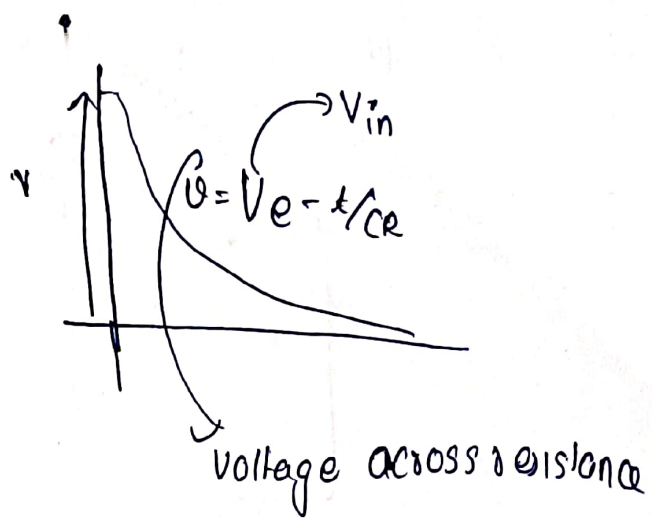find R from here $R = \frac{t}{C \log_e \left(\frac{V_0}{V} \right)}$



$$R = \frac{0.4343 t}{C \log_{10} \left(\frac{V_0}{V} \right)}$$

$\uparrow$ initial voltage
 $\downarrow$ final voltage




$$R = \frac{0.4343 t}{C \log_{10} \left(\frac{V}{V-E} \right)}$$

$\downarrow$ residual voltage

Limitations


→ Requires resistance of very high leakage resistance similar to R

② Mega Ohm bridge

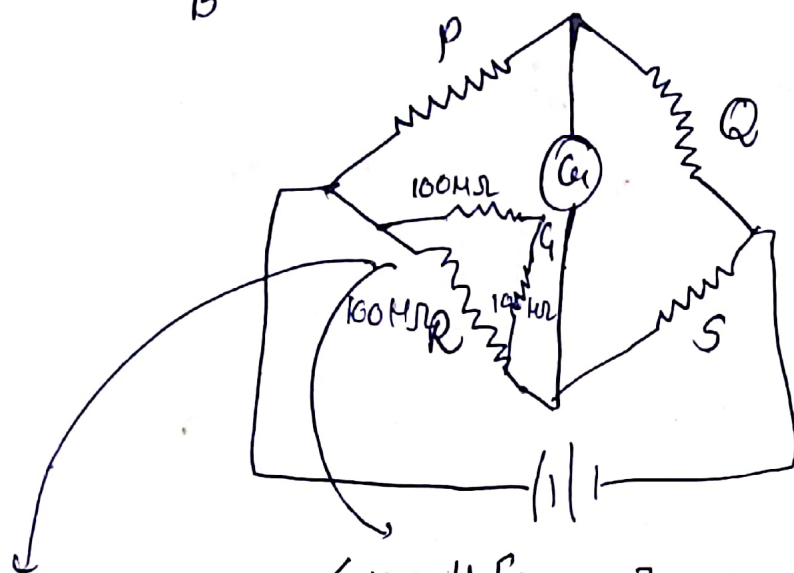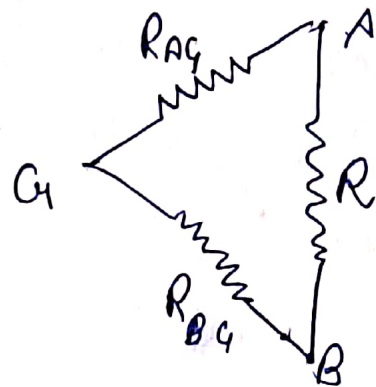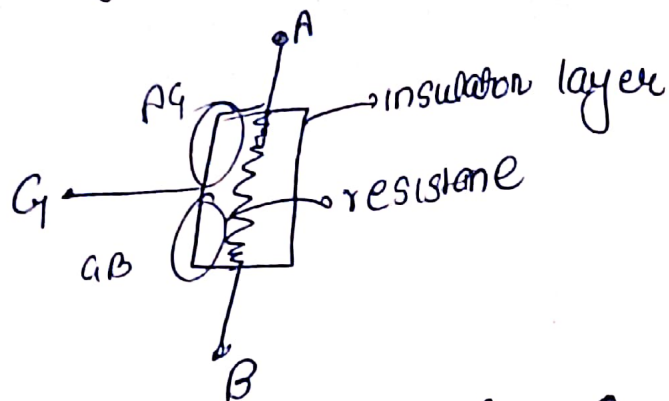


$$\text{measure} = \frac{100 \times 200}{300} = 67 \text{ M}\Omega$$
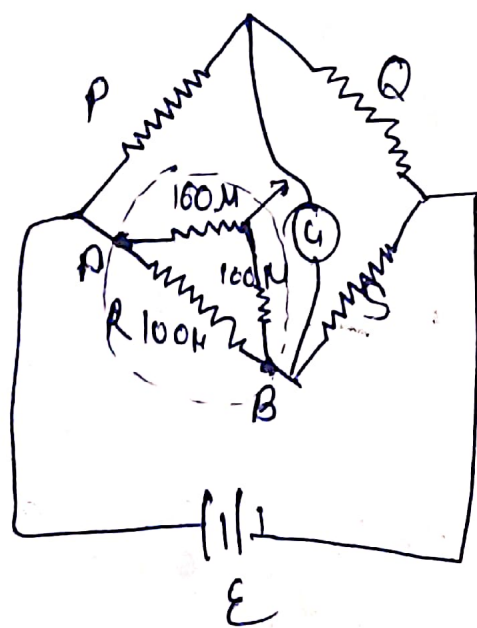
$$\angle 100 \parallel [200 \text{ M}\Omega] \angle 100 \text{ M}\Omega$$
 → so much error



→ In this case resistance R_{BG} is put in parallel with the galvanometer and thus it has no effect on balance because R_G is very low and will only affect the sensitivity of the galvanometer slightly the resistance

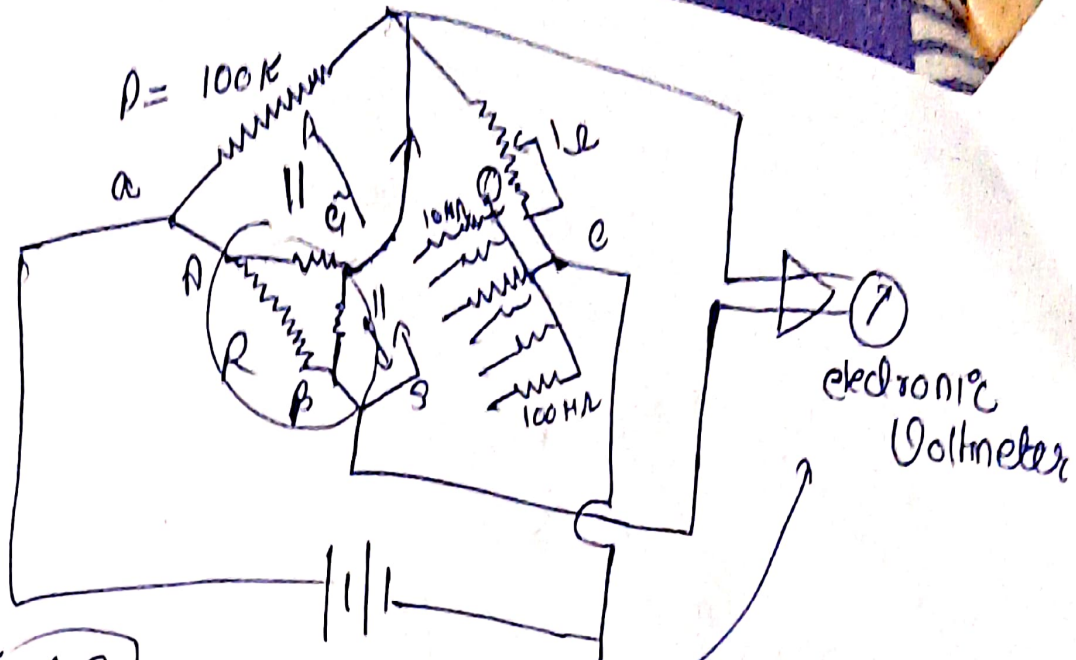this arrangement will give the correct value of R resistance



$$R = \frac{\rho S}{Q}$$

known

where it is 0


A.C. Bridges → capacitance

L, M, C, Q (measurement)

self inductance

Q-point

mutual inductance

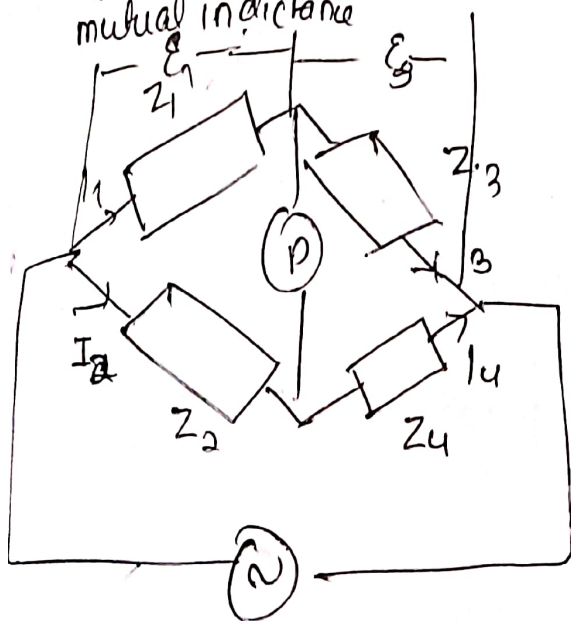

during balance


$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$

$$Z_1 L O, Z_4 L O_4 = Z_2 L O, Z_3 L O_3$$

equates Real and imaginary terms and we will get answer

(a) Measurement of L

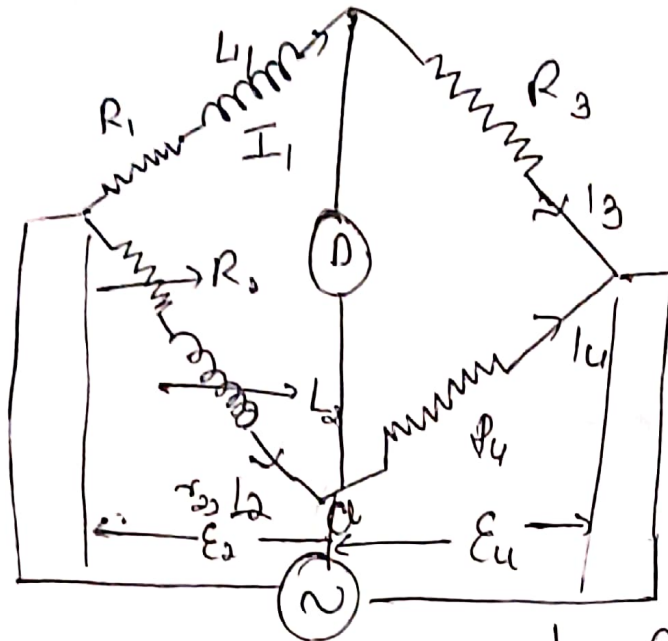1) Maxwell Inductance Bridge (unknown L, R)



L_1 = unknown inductance of Resistance R_1 .

L_2 → variable inductance of fixed resistance r_2 .

r_2 → variable resistance in series with L_2

R_3, R_4 → non inductive resistances

at balanced condition

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) R_4 = (R_2 + r_2 + j\omega L_2) R_3$$

$$\underbrace{R_1 R_4 + j\omega L_1 R_4}_{\text{real}} = \underbrace{(R_2 + r_2) R_3}_{\text{real}} + \underbrace{j\omega L_2 R_3}_{\text{imaginary}}$$

real

$$R_1 R_4 = (R_2 + r_2) R_3$$

$$\frac{R_1 R_4 - R_2 R_3}{R_3} = r_2$$



imaginary

$$\omega L_1 R_4 = \omega L_2 R_3$$

$$L_1 = \frac{R_3}{R_4} L_2$$

$$R_1 = \frac{R_3}{R_4} (R_2 + r_2)$$

resistance of unknown branch

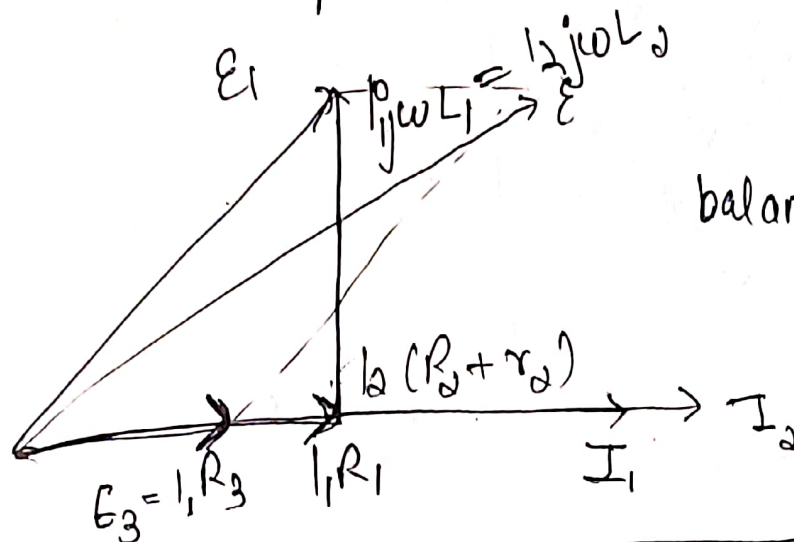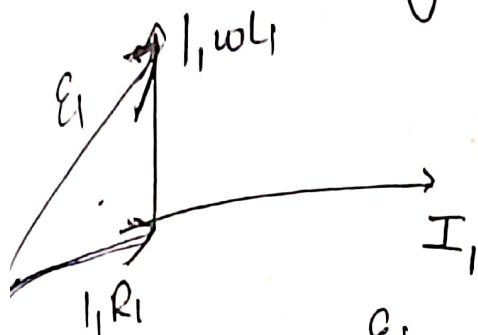

balanced condition

complex and
real y separate

$$E_3 = I_1 R_3$$

$$E_4 = I_2 R_4$$

$$I_1 R_1 = I_2 (R_2 + r)$$

in balanced $E_1 = E_2$ } (in phase)
 $E_3 = E_4$

$$E_3 = E_4$$

$$I_1 R_3 = I_2 R_4$$

$$E_1 = E_2$$


$$I_1 R_1 = I_2 (R_2 + r)$$

$$I_1 \omega L_1 = I_2 \omega L_2$$

$$E_1 + E_3 = E$$

for any bridge $\rightarrow \epsilon_1 + \epsilon_3 = \epsilon$
 $\epsilon_1 = \epsilon_2$ and $\epsilon_3 = \epsilon_4$ } in any bridge

Maxwell inductance Capacitance Bridge

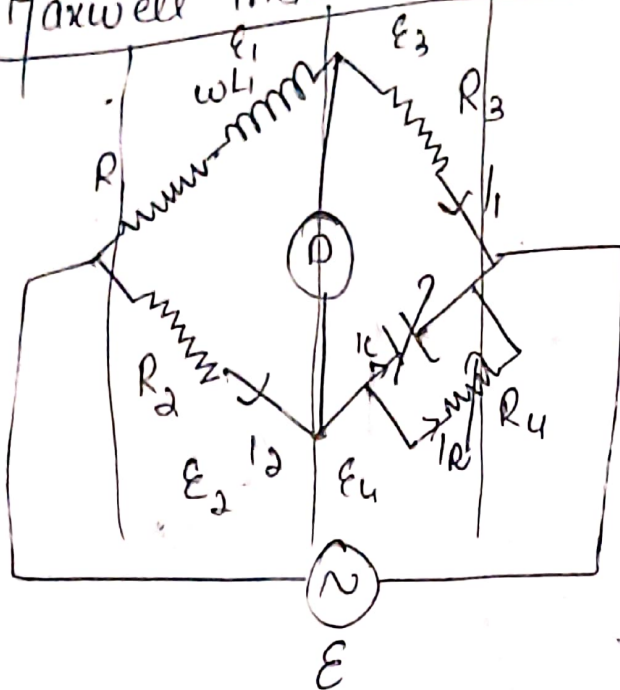

$(R_1, L_1) \rightarrow$ unknown

$L_1 =$ unknown inductance

$R_1 =$ " resistance associated with L_1

R_2, R_3, R_4 non inductive resistance

$C_4 \Rightarrow$ variable standard capacitance

$$Z_1 Z_4 = Z_2 Z_3 \quad Z_1 Z_4 = \underline{Z_2 Z_3}$$

$$(R_1 + j\omega L_1) \left(\frac{R_4}{j\omega C_4} \right) = R_2 R_3$$

$$R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega \frac{R_2 R_3 C_4}{R_4}$$

$$R_1 R_4 = R_2 R_3$$

$$R_1 = \frac{R_2 R_3}{R_4}$$

$$L_1 = R_2 R_3 C_4$$

Q factor $= \frac{\omega L_1}{R_1} = \frac{\text{reactance}}{\text{resistance}}$

$Q = \omega C_4 R_4$


advantages

- 1] Two balance equations are independent
- 2] frequency term doesn't appear

③ phasor

$E_1 = E_2, E_3 = E_4$


$E_1 + E_3 = E = E_2 + E_4$

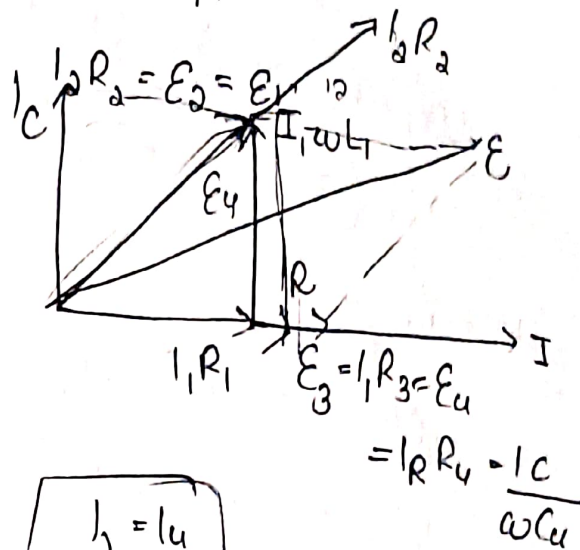

Anderson's Bridge

- accurate measurement of L
- advanced form of Maxwell's Inductance bridge
- unknown L is compared with C_{fix} .

Construction

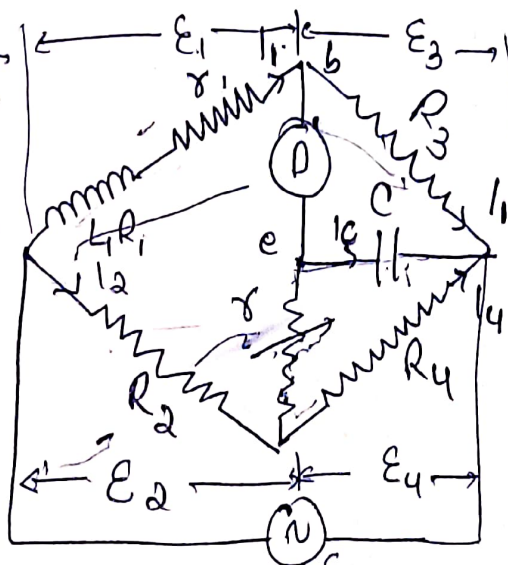

$L_1 \rightarrow$ self inductance to be measured

$R_1 \rightarrow$ resistance of self induct.

$r_1 \rightarrow$ resistance in series

$r_2, R_2, R_3, R_4 \rightarrow$ known non inductive resistances

$C =$ standard fixed capacitor

• Phasor Diagram

At balance condition,

$$I_1 = I_3 \text{ and } I_2 = I_C + I_4$$

$$I_1 R_3 = I_C \times \frac{1}{j\omega C} \quad (V_b = V_e)$$

$$I_C = -I_1 \omega C R_3$$

$$\rightarrow I_1 (R_1 + R_2 + j\omega L_1) = I_2 R_2 + I_C R_3$$

$$I_C \left(R_2 + \frac{1}{j\omega C} \right) = (I_2 - I_C) R_4$$

By substituting I_C

$$I_1 (R_1 + R_2 + j\omega L_1) = I_2 R_2 + I_1 j\omega C R_3 R_2$$

$$I_1 (R_1 + R_2 + j\omega L_1 - j\omega C R_3 R_2) = I_2 R_2$$

And

$$I_1 (R_3 + j\omega R_3 R_4 + j\omega C R_3 R_2) = I_2 R_4$$


imaginary and real

$$\rightarrow R_1 = R_2 \left(\frac{R_3 + R_4}{R_3} \right) = \frac{R_1 R_2}{R_3}$$

$$R_1 = \frac{R_2 R_3}{R_4} - R_2$$


$$L_1 = \frac{C R_3}{R_4} [4(R_4 + R_2) + R_2 R_4]$$

phasor →

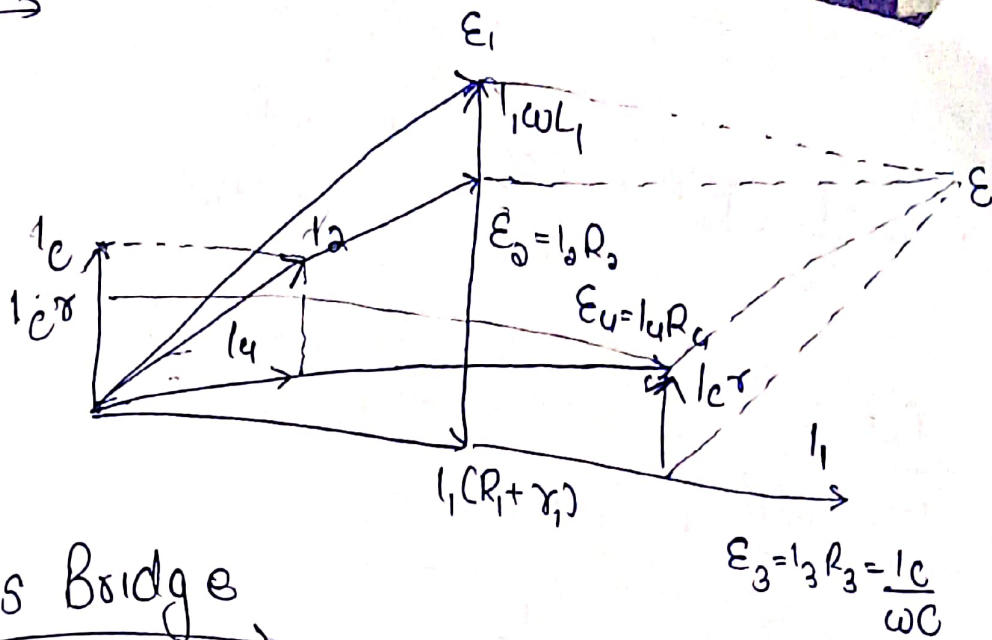

Hay's Bridge

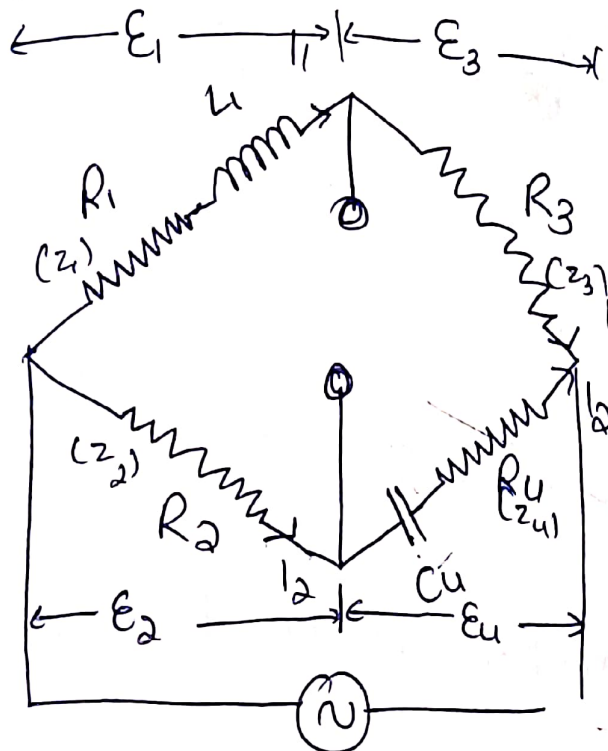- determining L
- advanced form of Maxwell's bridge
- Maxwell → medium Q
- Hay's → high Q



L_1 → unknown inductance with resistance R_1
 R_2, R_3, R_4 → known non-inductive resistance
 C_4 → standard capacitor

$$E_1 + E_3 = E$$

$$E_1 = E_2 \quad E_3 = E_4$$

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4} \rightarrow \frac{R_1 + j\omega L_1}{R_2} = \frac{R_3}{R_4 - \frac{j}{\omega C_4}}$$

$$\left(R_1 R_4 + \frac{\omega L_1}{C_4} \right) + j \left(\omega L_1 R_4 - \frac{R_1}{\omega C_4} \right) = R_2 R_3$$

Separating

$$R_1 R_4 + \frac{L_1}{C_4} = R_2 R_3$$


and $L_1 = - \frac{R_1}{\omega^2 R_4 C_4}$

$$L_1 = \frac{R_2 R_3 C_4}{1 + \omega^2 R_4^2 C_4^2}$$

$$R_1 = \frac{\omega^2 C_4^2 R_2 R_3 R_4}{1 + \omega^2 R_4^2 C_4^2}$$

$$Q = \frac{\omega L_1}{R_1} = \frac{1}{\omega^2 C_4 R_4}$$

Phasor

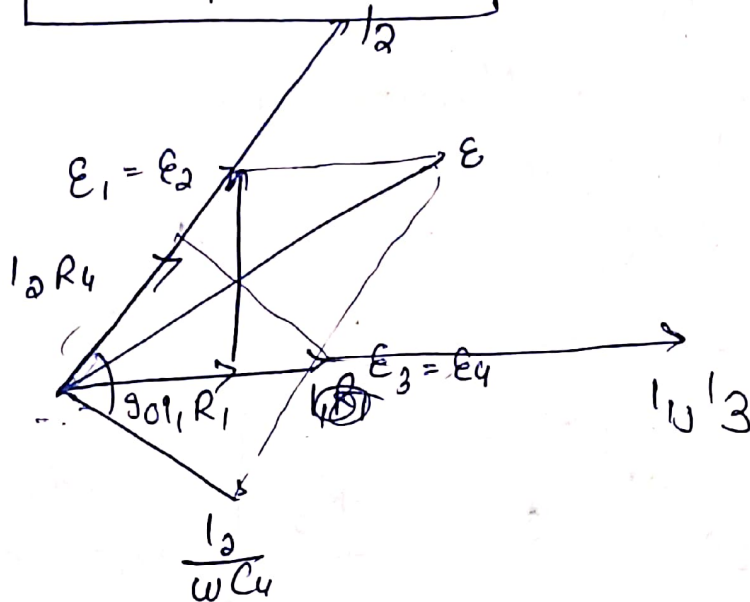


$$Q \propto \frac{1}{\omega}$$

frequency will affect Q

Coil Q higher $\rightarrow$ this method will not be suitable

* Owen's Bridge

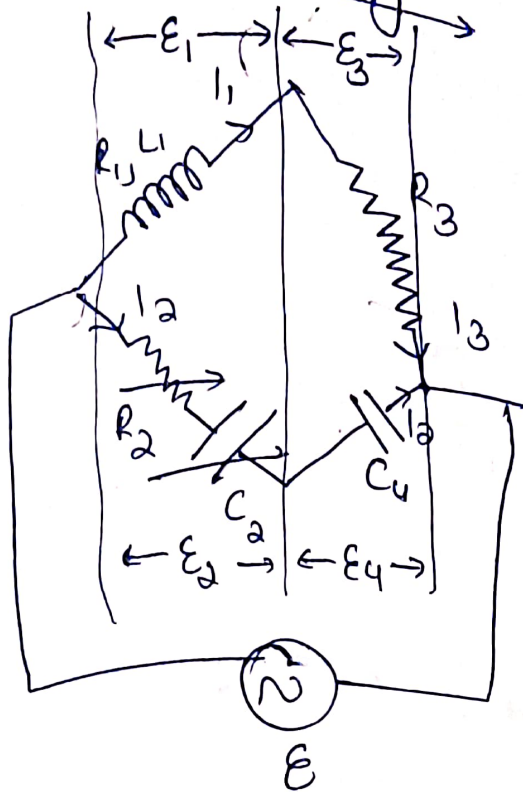

$$\frac{R_1 + j\omega L_1}{R_2 + \frac{j}{\omega C_2}} = \frac{R_3}{R_4 + \frac{j}{\omega C_4}}$$

$$(R_1 + j\omega L_1) \left(\frac{j}{\omega C_4} \right) = R_3 \left(R_2 - \frac{j}{\omega C_2} \right)$$

$$-\frac{jR_1}{\omega C_4} + \frac{L_1}{C_4} = R_3 R_2 - \frac{jR_3}{\omega C_2}$$

$$\frac{L_1}{C_4} - \frac{jR_1}{\omega C_4} = R_3 R_2 - \frac{jR_3}{\omega C_2}$$

$$\frac{L_1}{C_4} = R_3 R_2$$


$$L_1 = R_3 R_2 C_4$$


$$\frac{R_1}{\omega C_4} = \frac{R_3}{\omega C_2}$$

$$R_1 = \frac{C_4 R_3}{C_2}$$

different balanced condⁿ easy


Phasor →

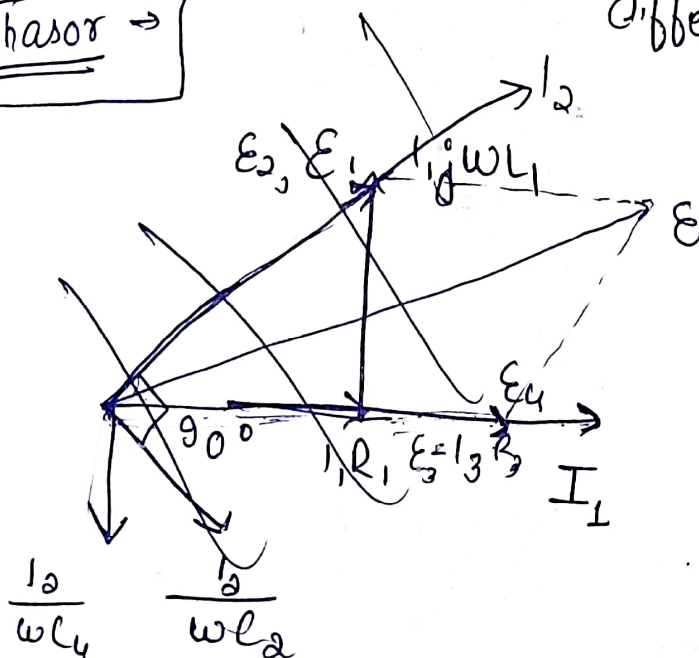

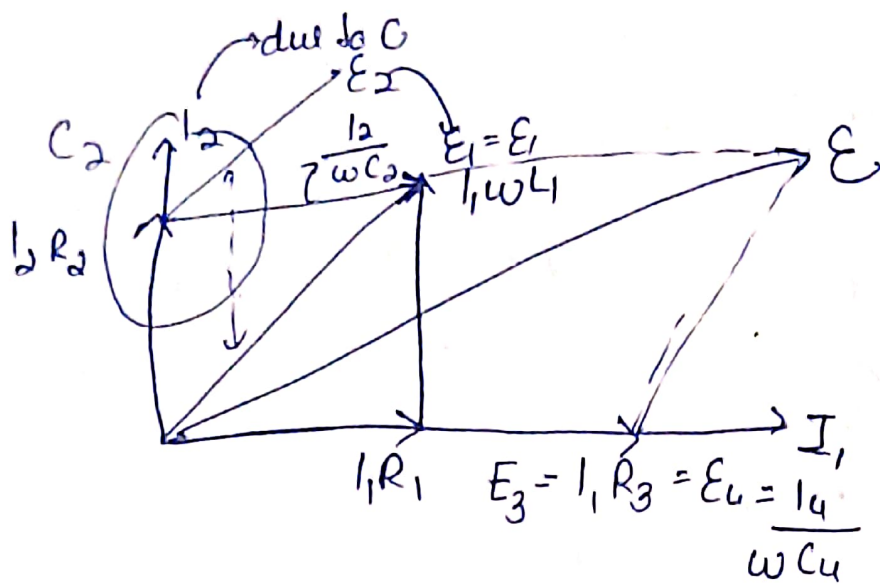

* Measurement of Capacitance

i) De sauty Bridge

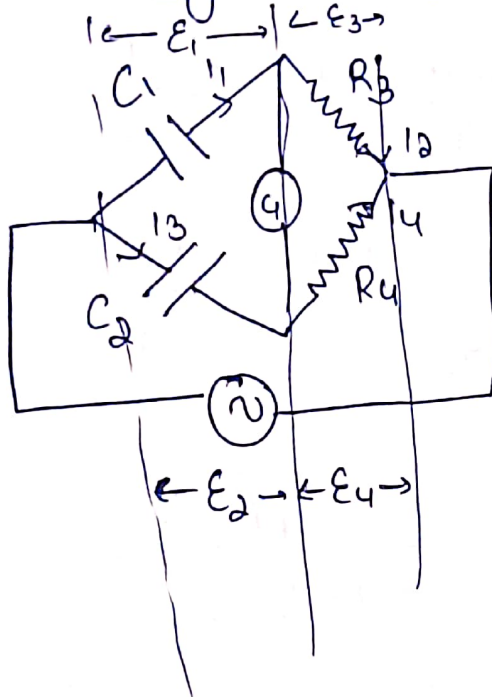

$C_1 \rightarrow$ determined

$C_2 \rightarrow$ standard capacitance

$R_3, R_4 \rightarrow$ non inductive R

during balance

$$\frac{1}{j\omega C_1} R_4 = \frac{1}{j\omega C_2} R_3$$


$$C_1 = \frac{C_2 R_4}{R_3}$$

$C_1, C_2 \rightarrow$ no dielectric loss
if present

ii) modified de Sauty Bridge

r_1, r_2 cause of
dielectric losses

R_1, R_2, R_3, R_4 standard resistors

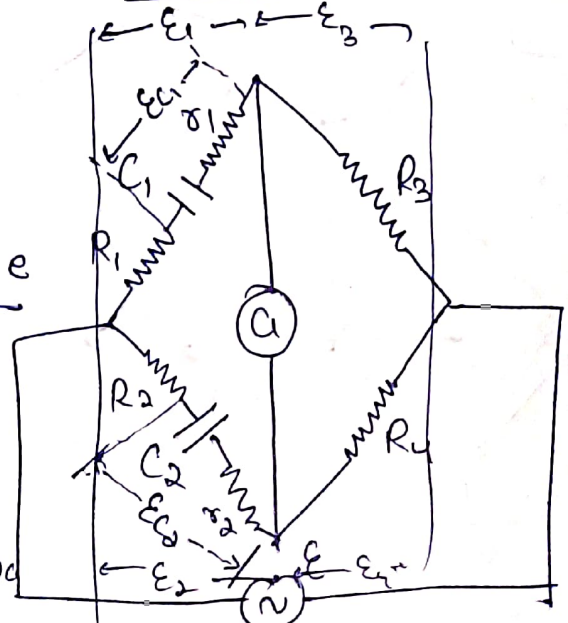

$$\left(R_1 + r_1 + \frac{1}{j\omega C_1} \right) R_4 = \left(R_2 + r_2 + \frac{1}{j\omega C_2} \right) R_3$$

$$\boxed{\frac{C_1}{C_2} = \frac{R_2 + r_2}{R_1 + r_1} = \frac{R_4}{R_3}}$$


Dissipation factor

$$D_1 = \tan \delta_1 = \omega C_1 r_1$$

$$D_2 = \tan \delta_2 = \omega C_2 r_2$$

$$\frac{C_1}{C_2} = \frac{R_2 + r_2}{R_1 + r_1} = \frac{R_4}{R_3} \rightarrow C_1 R_1 + C_1 r_1 = C_2 R_2 + C_2 r_2$$

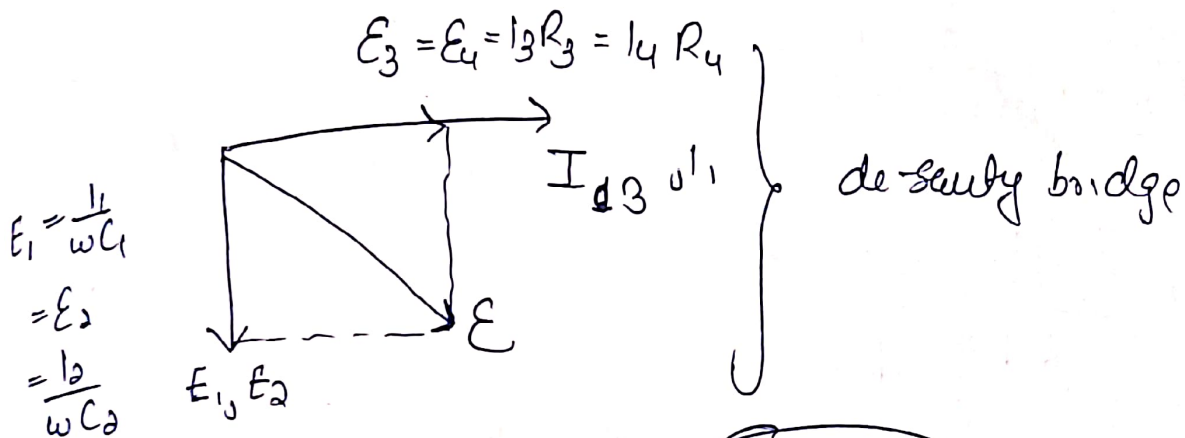
$$D_1 - D_2 = \omega C_2 \left(\frac{R_1 R_4}{R_3} - R_2 \right)$$



*modified


$$\frac{C_1}{C_2} = \frac{R_2 + r_2}{R_1 + r_1}$$

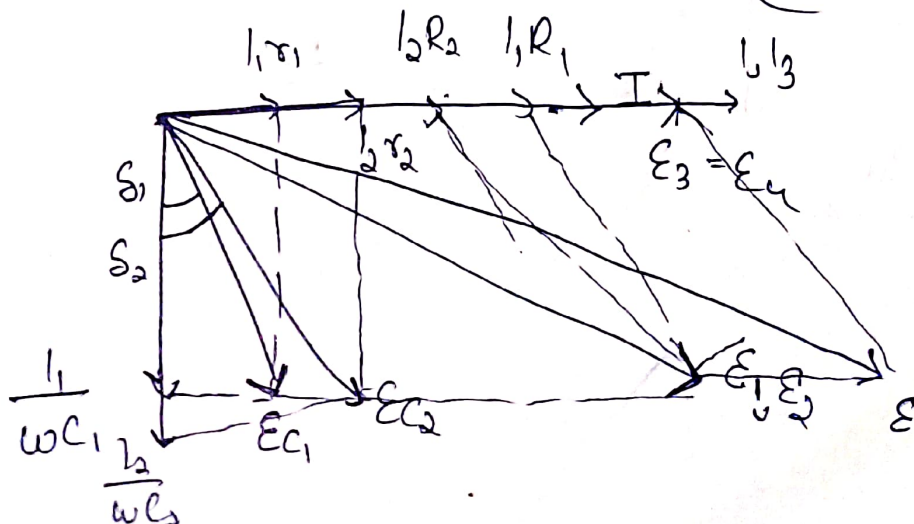ratio
 $(I_1 \rightarrow I_2)$ same phase



2) Shering Bridge

Shering Bridge

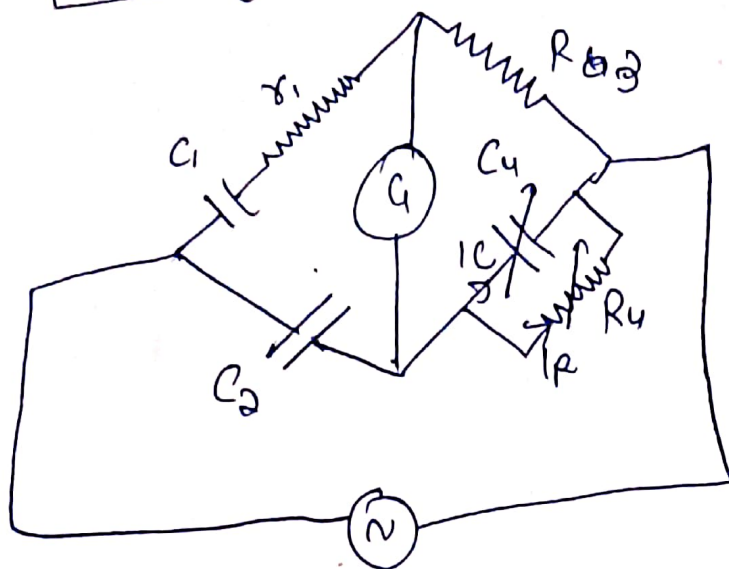

$C_1 \rightarrow$ to be determined

loss $r_1 \rightarrow$ series

$C_2 \rightarrow$ standard capacitor (A.C.)

$R_3, R_4 \rightarrow$ non inductive resistance


$C_4 \rightarrow$ Variable capacitor

$$\left(r_1 + \frac{1}{j\omega C_1} \right) \left(\frac{R_4}{1 + j\omega C_4 R_4} \right) = R_3 \frac{1}{j\omega C_2}$$

$$\boxed{r_1 = \frac{R_3 C_4}{C_2}}$$


$$\boxed{C_1 = C_2 \left(\frac{R_4}{R_3} \right)}$$

$$D_1 = \tan \delta_1 = \omega C_1 r_1$$

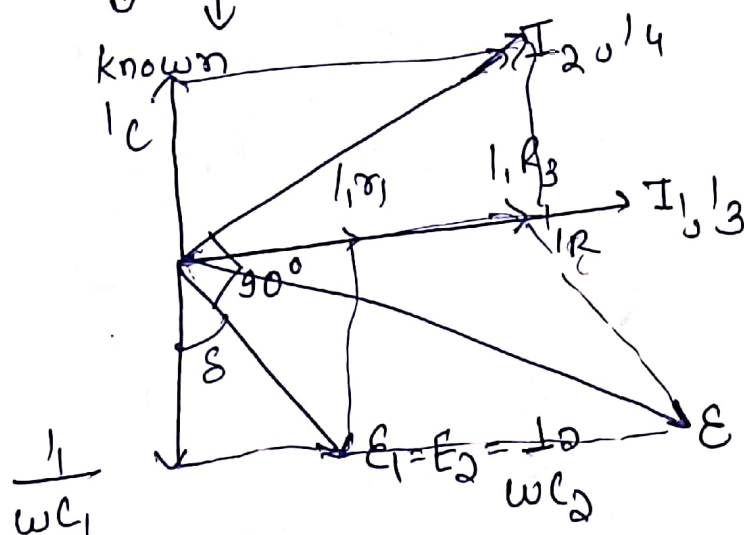

frequency measurement

i) Wein's Bridge

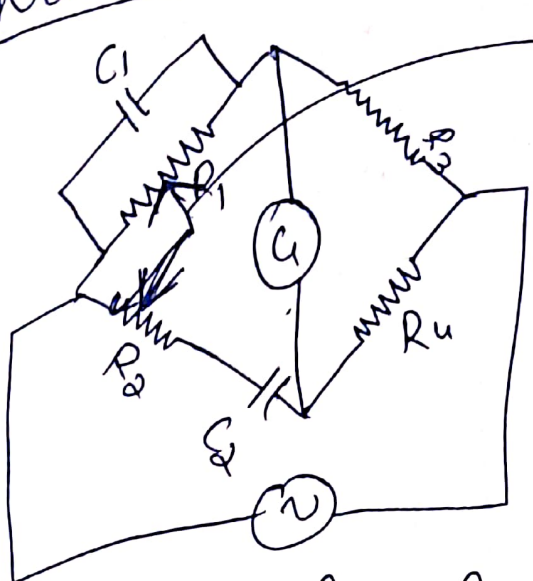

mechanical linkage

→ Same variation R_1 and R_2

$$\left(\frac{R_1}{1+j\omega C_1 R_1} \right) R_4 = R_3 \left(R_2 - \frac{j}{\omega C_2} \right)$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} = \frac{C_2}{C_1}$$

$$\omega C_1 R_2 - \frac{1}{\omega C_2 R_1} = 0$$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$


Measurement of mutual inductance

Case 1^o




$$V_1 = L_1 + L_2 + 2M$$

Case 2^o

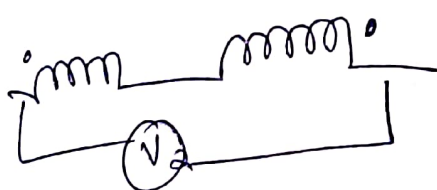


$$V_2 = V_1 + L_2 - 2M$$

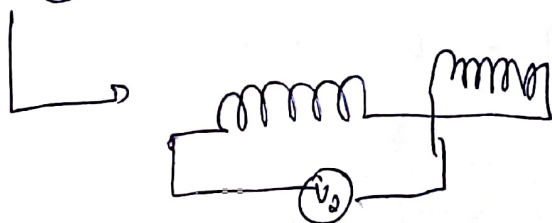


$$M = \frac{1}{4} (V_1 - V_2)$$

simplest method

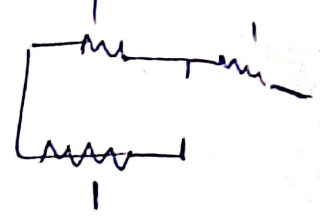

ii] Heaviside mutual inductance bridge

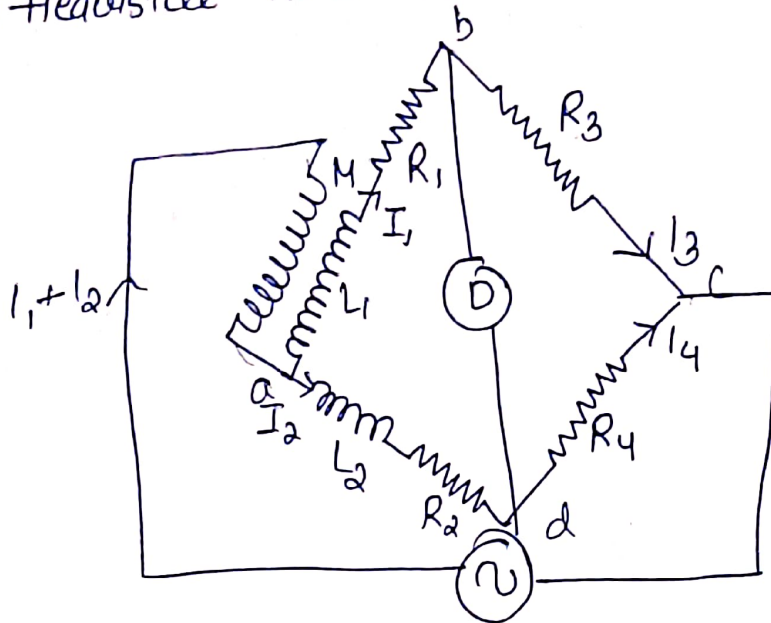

M = unknown M
 L_1 = self inductance
 secondary coil of
 mutual inductance

L_2 = known self inductance
 R_1, R_2, R_3, R_4 = non inductive
 resistances.

$$I_1 R_3 = I_2 R_4$$

$$V_{abc} = V_{ode}$$

$$(I_1 + I_2) j\omega M + I_1 (R_1 + R_3 + j\omega L_1) = I_2 (R_2 + R_4 + j\omega L_2)$$

$$\frac{1}{2} \left(\frac{R_4}{R_3} + 1 \right) j\omega M + \frac{R_4 I_2}{R_3} (R_1 + R_3 + j\omega L_1) = \frac{1}{2} (R_2 + R_4 + j\omega L_2)$$

$$\left(\frac{R_4}{R_3} + 1 \right) j\omega M + \frac{R_4}{R_3} (R_1 + R_3 + j\omega L_1) = R_2 + R_4 + j\omega L_2$$

$$j \left(\frac{R_4}{R_3} + 1 \right) \omega M + \omega L_1 \frac{R_4}{R_3} = \omega L_2$$

$$\frac{R_4 M}{R_3} = L_2 - \frac{L_1 R_4}{R_3}$$

$$M = \frac{R_3 L_2 - L_1 R_4}{R_3 + R_4}$$

$$M = \frac{L_2 - L_1}{2}$$

This method can also be used for finding self inductance

$$L_2 = \frac{M(R_3 + R_4) + R_4 L_1}{R_3}$$

Q] An Owen's bridge used to measure the properties of steel sheet (L, R) frequency is 2kHz at balance arm ab is the test arm bc $R_3 = 100\Omega$ arm cd = capacitor $C_4 = 0.1\mu F$ arm da $R_2 \rightarrow 834\Omega$ is series with capacitor having value of $0.124\mu F$ derive balance condition and calculate the effective impedance of specimen

$$Z \times X_C = R_3 \times Z_2$$

$$Z = \frac{100 \times \sqrt{834^2 + \left(\frac{10^6}{2\pi \times 2 \times 10^3 \times 0.124} \right)^2}}{\frac{10^6}{0.1}}$$

$$Z = \frac{100 + \sqrt{834^2 + 79.57^2}}{\frac{10^6}{0.1}} = \frac{100 + 837.79}{\frac{10^6}{0.1}}$$

$$= \frac{937.79}{\frac{10^6}{0.1}}$$

$$= 0.937\mu H$$

Q.2] $ab \rightarrow$ choke coil R_1, L_1

$bc \rightarrow$ non inductive resistance R_3

$cd \rightarrow C_4$ (microcondensor) non inductive Resistance R_4 in series
dielectric

$da \rightarrow$ non inductive resistance R_2

$f = 500 \text{ Hz}$ balance obtained


$$R_3 = 2410 \Omega$$

$$R_3 = 750 \Omega$$

$$C_4 = 0.35 \mu\text{F}$$

$$R_4 = 64.5 \Omega$$

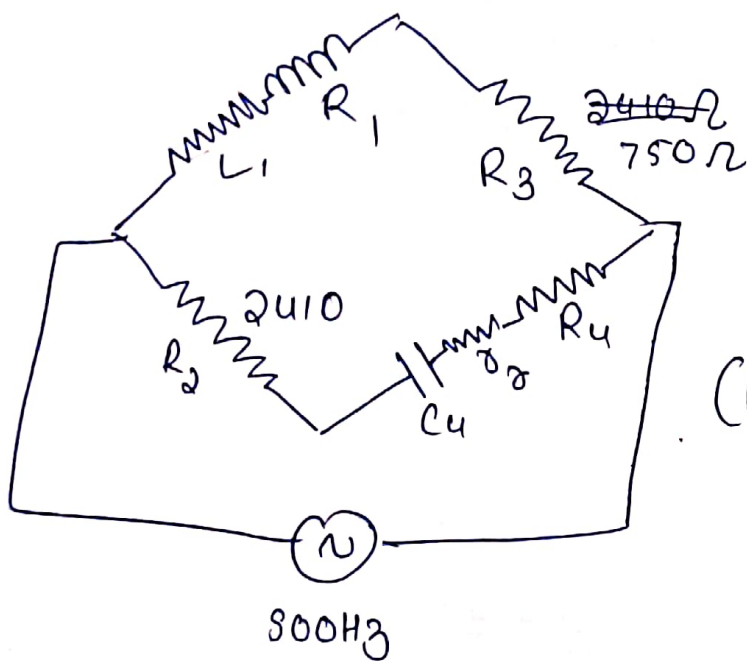Series resistance of capacitor is 0.4Ω calculate resistance and inductance of choke coil supply a and c.



$$(R_1 + j\omega L_1)(R_4 + R_4) - \frac{j}{\omega C_4} = R_3 R_2$$

$$(R_1(R_4 + R_4) + \frac{L_1}{C_4}) + j(\omega L_1(R_4 + R_4) - \frac{R_1}{\omega C_4}) = R_3 R_2$$

$$R_1(R_4 + R_4) + \frac{L_1}{C_4} = R_3 R_2$$

$$i) \quad R_1, 64.9 + L_1 (2857142) = 1807500$$


$$\omega(R_4 + R_4)L_1 - \frac{1}{\omega C_4} R_1 = 0$$

$$R_1 = 141.1 \Omega$$

$$L_1 = 0.63 \text{ mH}$$

$$-809.45 R_1 + 203889 L_1 = 0 \quad ii)$$

① Magnetic Measurements

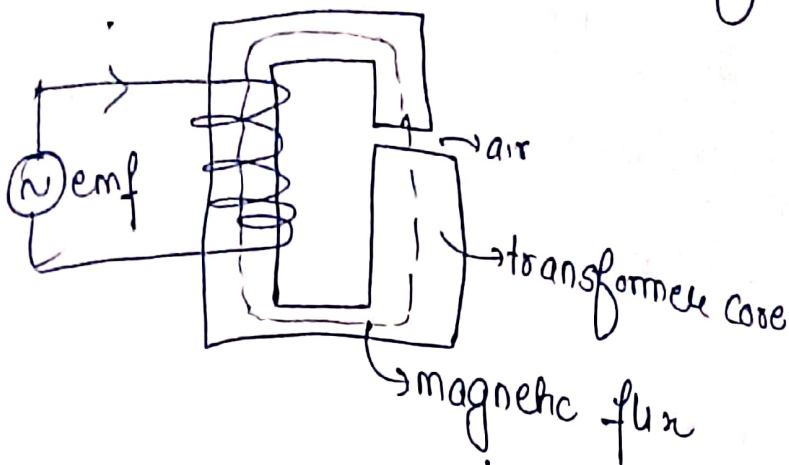

$B \rightarrow$ flux density / magnetic field strength

$H \rightarrow$ magnetising force

$I \rightarrow A$

$\mathcal{E} \rightarrow V$

$\frac{\mathcal{E}}{I} \rightarrow \text{Resistance}$


$B \rightarrow T / \text{or } Wb/m^2$

$H \rightarrow \text{produce } B \rightarrow AT \text{ (mmf)}$

$\rho \rightarrow \text{Reluctance} \rightarrow \frac{H}{B}$

$\rightarrow$ determine the B-H curve / hysteresis loop of a specimen

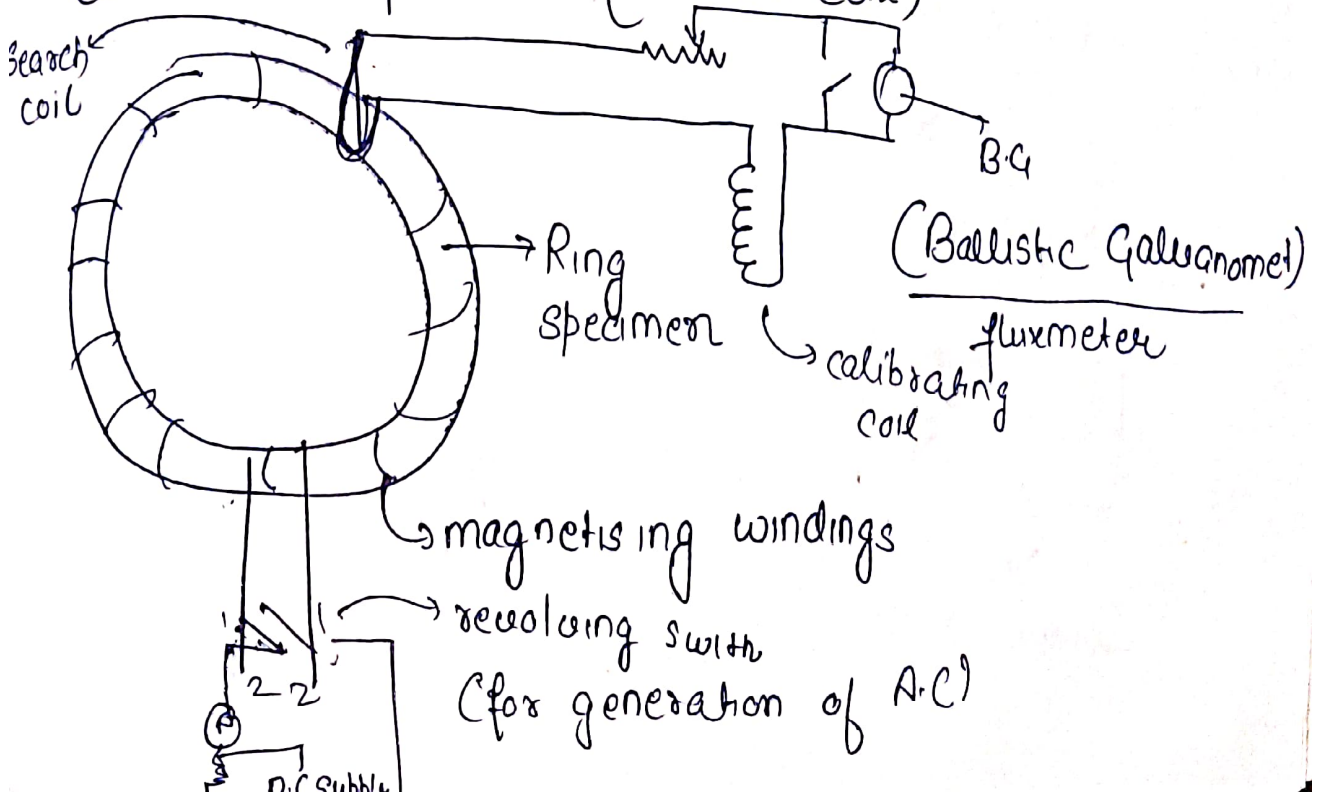$\rightarrow$ coil over specimen (search coil)



The current through the magnetising coil is reversed and the flux linkages in the search coil change inducing an emf which sends a current through the fluxmeter or ballistic galvanometer indicating its value

let $\phi \rightarrow$ flux linking the search coil

$R \rightarrow$ resistance of ballistic galvanometer circuit

$N \rightarrow$ Number of turns in search coil

$t \rightarrow$ time taken to reverse the flux

$$e = N \frac{d\phi}{dt} \quad e = \frac{2N\phi}{t} \quad \text{flux changing 2 times in unit time}$$

$$i = \frac{2N\phi}{tR} \quad Q = \frac{2N\phi}{R}$$

Charge induced in the BG

$$= K_g Q_1$$

$$\frac{2N\phi}{R} = K_g Q_1$$

$$\phi = \frac{K_g Q_1 R}{2N}$$

linear scale

$$B = \frac{\phi}{A}$$

$\hookrightarrow$ Gross sectional area Search Coil
Magnetising

Correction for the air flux

loss of flux in air



$$B'A_s = BA_s + \mu_0 H (A_c - A_s)$$


Observed flux true flux

losses in air space between magnetising and search coil

$$B = B' - \mu_0 H \left(\frac{A_c}{A_s} - 1 \right)$$


* Measurement of H (magnetising force)

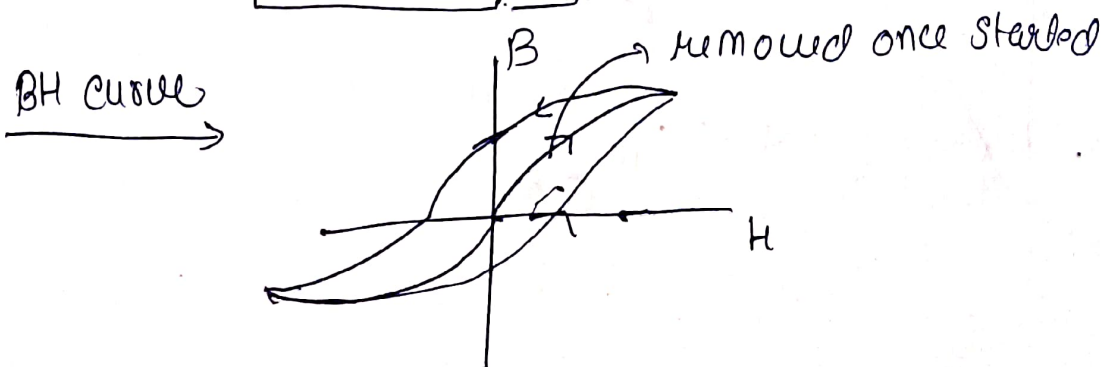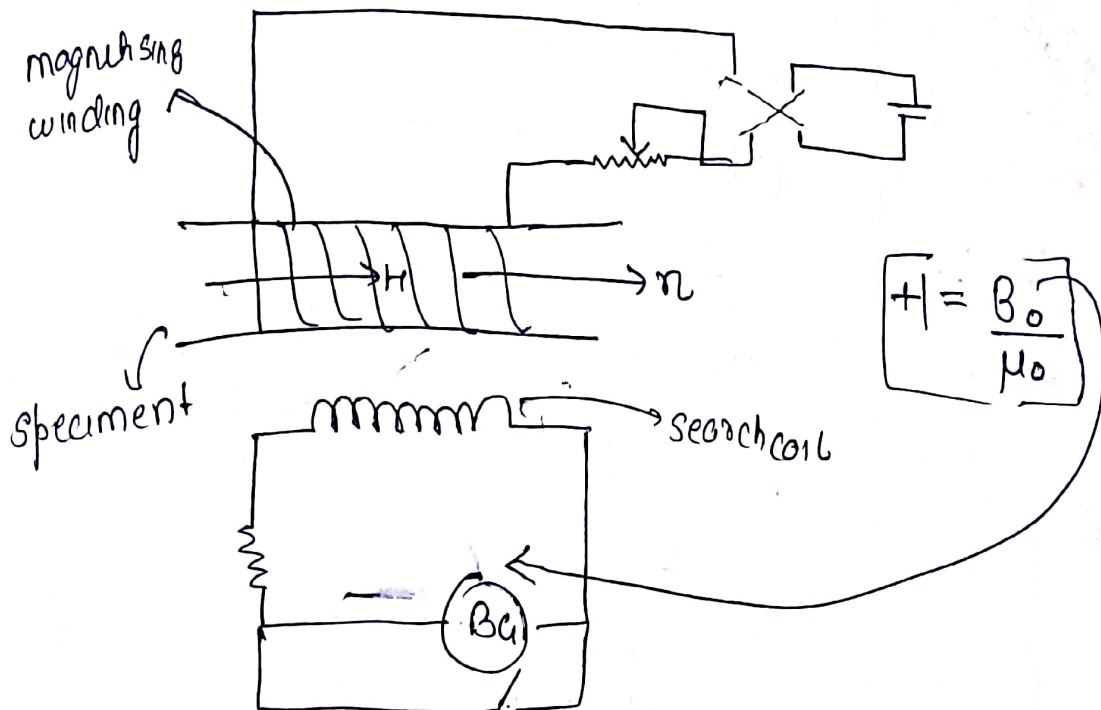

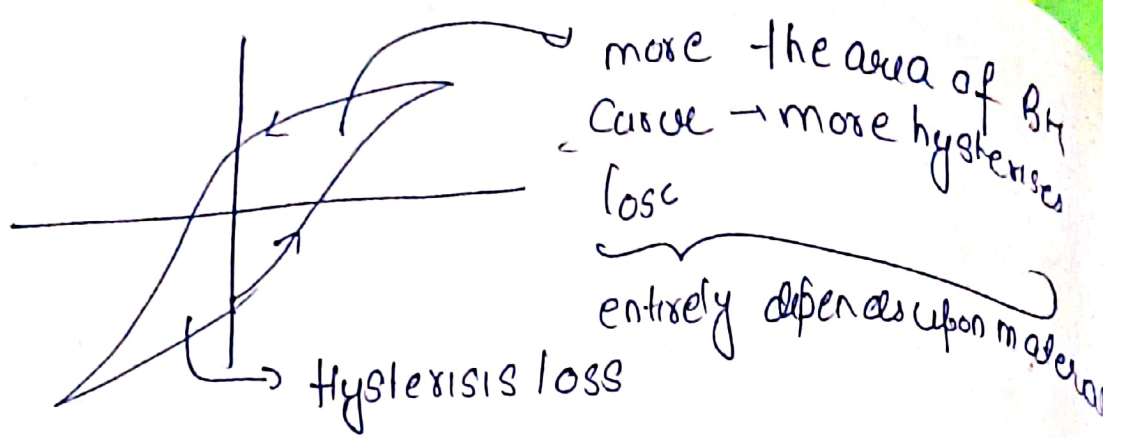

① Step by step method

① method of reversal

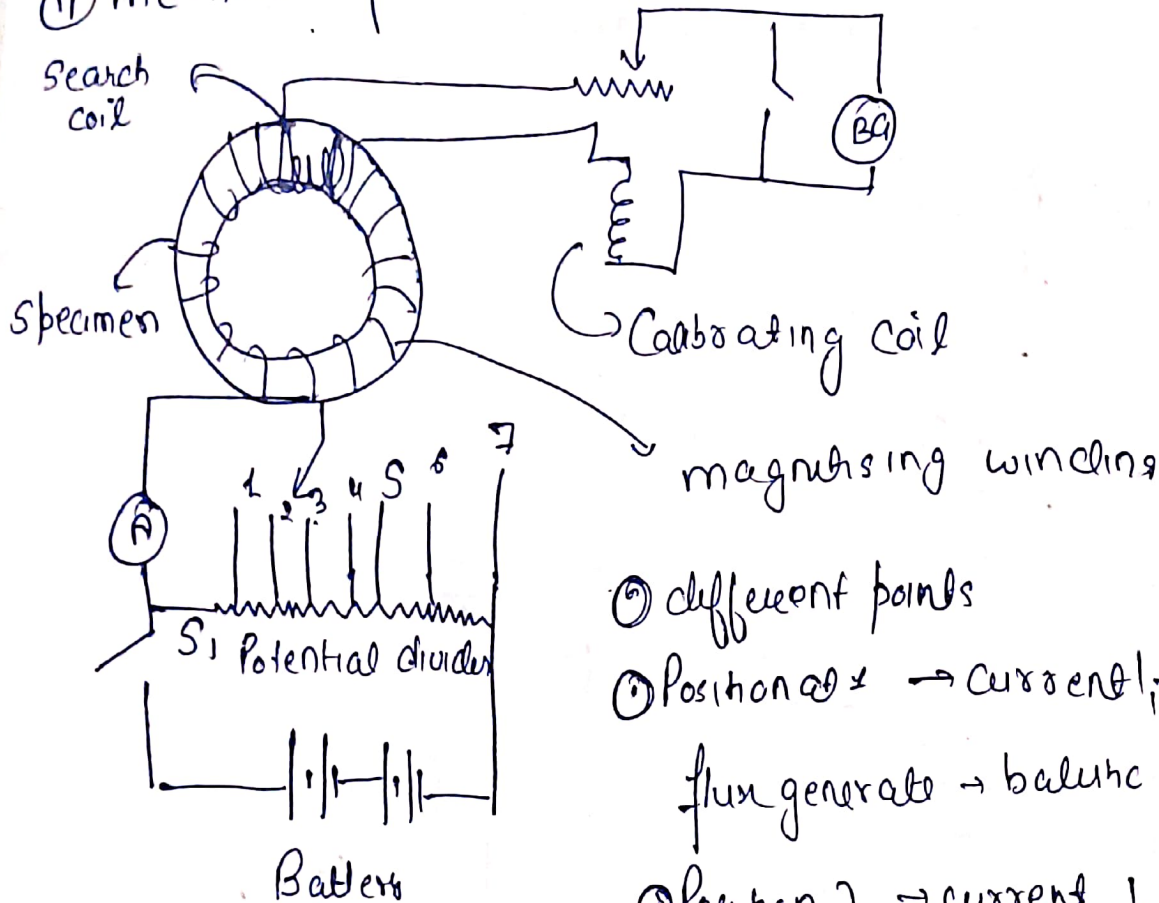

① different points


① Position 1 $\rightarrow$ current $I_1 \rightarrow H_1$
flux generated $\rightarrow$ ballistic galvanometer

① Position 2 $\rightarrow$ current $I_2 \rightarrow H_2 \rightarrow \phi_2$
 $\rightarrow$ ballistic galvanometer

① Then again spring back to 1 from:


① at point C reverse battery to reverse

① then again repeat the same process

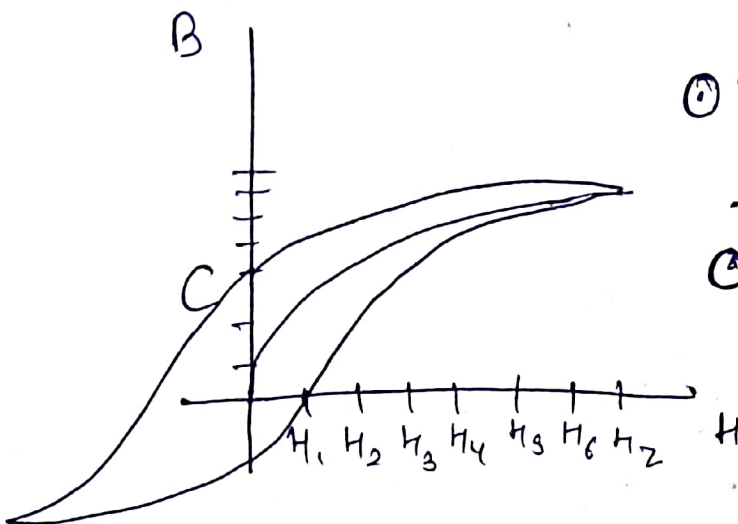

Increase $\rightarrow$ dec $\rightarrow$ reverse battery
 Increase neg potential $\rightarrow$ dec battery

2] Method of reversal

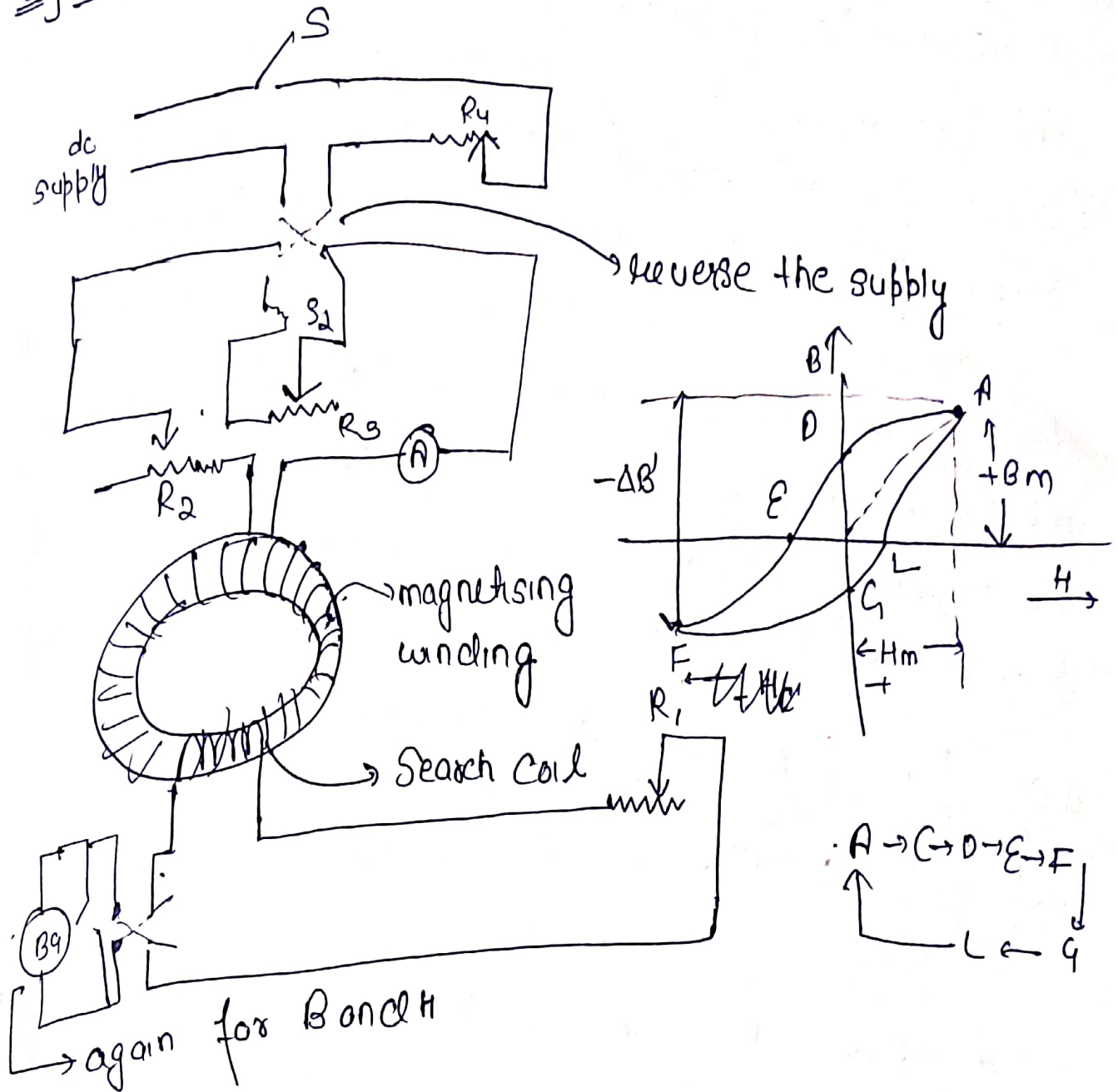

(c) flux density is measured at each step from the maximum value $+B_m$ to some lower value. The connection R_1, R_2, R_4 in the magnetizing winding and galvanometric winding R_3 a variable resistance which is connected across the magnetization winding via switch S_2 .

∴ R_s and R_i will be of B and H

Q] A ferromagnetic material is tested with help of a permeameter provided with the coil wound over the specimen, this coil is known as B coil (Search coil) and another coil is wound near surface of the coil known as H coil. These two coil are connected to separate ballistic galvanometer having constant of $25 \times 10^{-6} \text{ wb/tum/scale div}$. The testing is done by reversing the current of the magnetising winding the reading of Ballistic gale. connected to B coil $\rightarrow 100 \text{ div}$ H coil $\rightarrow 10 \text{ div}$ (B, ϕ)

coil	N	Area
B	100	$50 \times 10^{-6} \text{ m}^2$
H	10,100	$3 \times 10^{-6} \text{ m}^2$

- find the flux density and magnetising force in the specimen
- find relative permeability of the specimen.

$\phi \rightarrow$ flux $N \rightarrow$ number of turn

$$\phi \Rightarrow \text{flux linkage} = N\phi$$

$$\text{due to reversal} = 2N\phi$$

$$\text{flux linkage with B coil} = K_p \frac{\phi}{\phi}$$

$$2N\phi = K_p \phi$$

$$\phi = \frac{K_p \phi}{2N}$$

∴ R_s and R_l will be of B and H

Q] A ferromagnetic material is tested with help of a permeameter provided with the coil wound over the specimen, this coil is known as B coil (Search coil) and another coil is wound near surface of the coil known as H coil. These two coils are connected to separate balance galvanometer having constant of $25 \times 10^{-6} \text{ Wb/tum/scale div}$. The testing is done by reversing the current of the magnetising winding the reading of Balance galvanometer connected to B coil $\rightarrow 100 \text{ div}$ H coil $\rightarrow 100 \text{ div}$ (B, ϕ)

Coil	N	Area
B	100	$50 \times 10^{-6} \text{ m}^2$
H	10,100	$8 \times 10^{-6} \text{ m}^2$

- find the flux density and magnetising force in the specimen
- find relative permeability of the specimen.

$\phi \rightarrow$ flux $N \rightarrow$ number of turn

$\phi \Rightarrow$ flux linkage $= N\phi$

due to reversal $= 2N\phi$

flux linkage with BG $= \frac{K_p \theta_1}{\phi}$

$$2N\phi = K_p \theta_1$$

$$\phi = \frac{K_p \theta_1}{2N}$$

$$B = \frac{\mu_0 \theta_1}{2NA}$$

$$= \frac{25 \times 10^{-6} \times 100}{2 \times \cancel{60 \times 80 \times 10^{-6}}} = 0.25 \text{ Wb/m}^2$$

4 coil $\rightarrow$ first B

$$B = \frac{\mu_0 \theta_1}{2NA} = \frac{25 \times 10^{-6} \times 10^5}{2 \times 10,000 \times 5 \times 10^{-6}}$$

$$B = 0.0025 \text{ Wb/m}^2$$

$\hookrightarrow$ in 4 coil

$$H = \frac{B}{\mu_0} = \frac{B}{4\pi \times 10^{-7}} = 2000 \text{ A/m}$$

2000 AT

$$\underline{\underline{\mu_r}} = \frac{B}{\mu_0 H} = \frac{0.25}{4\pi \times 10^{-7} \times 2000} = \boxed{\mu_r = 100}$$

of the B coil